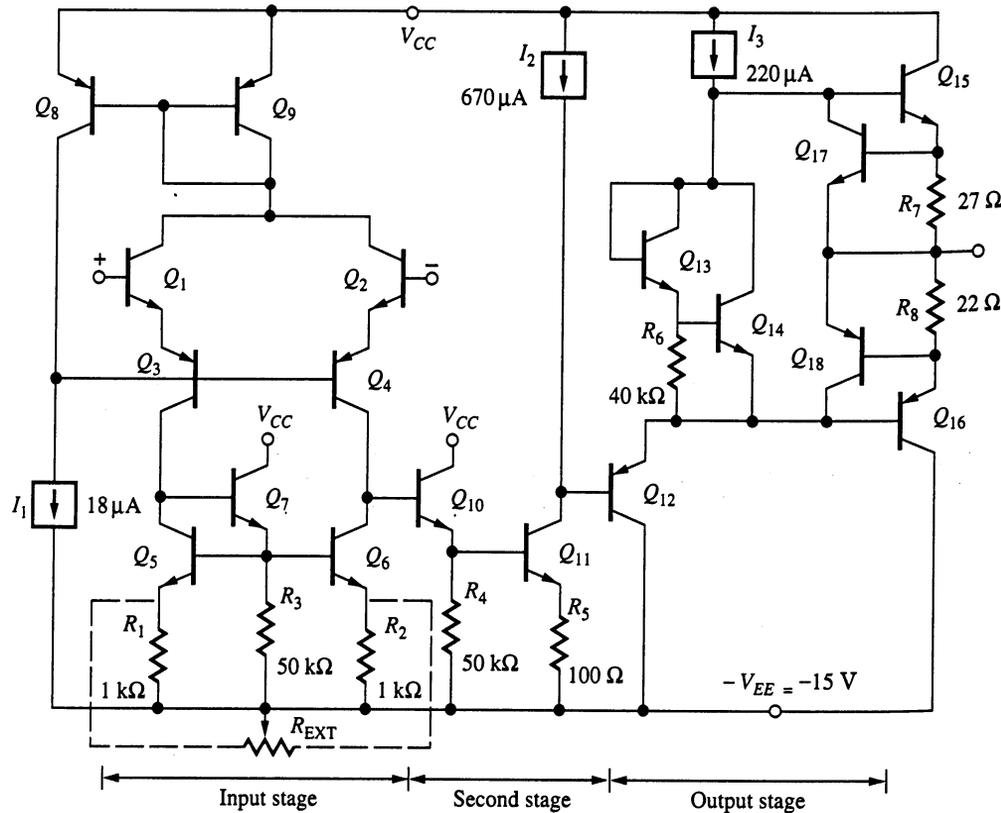


# 741 Voltage Gain



□ Analysis strategy:

1) Find Norton equivalent of input stage.

2) Couple this with 2-port representation of 2nd stage.