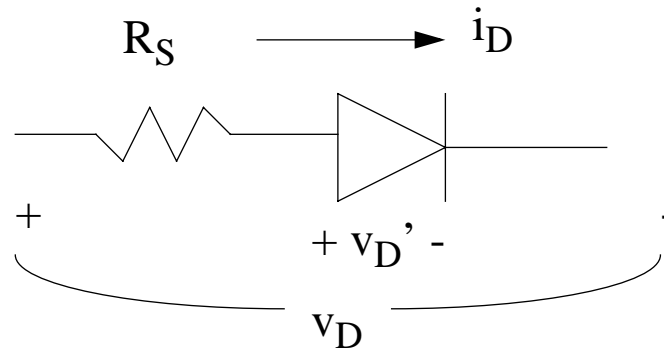


Diode SPICE Model

- DC equivalent circuit used for SPICE model of pn diode:



- i - v characteristics modeled by 2 parameters: the saturation current (I_S) and the ideality factor (N)

$$i_D = I_S \left(e^{v_{D'}/NV_{th}} - 1 \right)$$

Diode SPICE Model

- Ideality factor accounts for generation-recombination in the depletion region of the diode (ignored in our derivation for i_D)
- Usual range for N is 0.5 - 1
- R_S is the series resistance of the quasineutral p and n regions plus the ohmic contacts
- True junction voltage given by: $v_D' = v_D - i_D R_S$
- Charge storage in the diode is modeled by the depletion capacitance C_j

Diode SPICE Model

- Complete list of SPICE diode model parameters:

Parameter	Symbol	SPICE name	Units	Default
Saturation current	I_0 or I_S	IS	A	10^{-14}
Emission coefficient	n or N	N	-	1
Series resistance	R_S	RS	Ω	0
Built-in voltage	V_{bi} or ϕ_j	VJ	V	1
Junction Capacitance	C_{j0}	CJ0	F	0
Grading coefficient	m	M	-	0.5
Transit time	τ_t	TT	s	0
Breakdown voltage	V_{BD}	BV	V	∞
Reverse current at breakdown	I_{BD}	IBV	A	10^{-10}

Diode SPICE Model

- Diode included in circuit using the following line:

```
DXXX NP NN DNAME
```

where: XXX = diode number

NP, NN = positive and negative diode nodes

DNAME = model name

- Diode model requires a .MODEL statement:

```
.MODEL DNAME TYPE (PNAME1=PVAL1 PNAME2=PVAL2 ...)
```

where: TYPE D

PNAME1 = is model parameter 1, with value PVAL1, etc.

Example:

```
.MODEL DMOD D (IS=1E-17 RS=20 CJO=1P TT = 50N)
```

Brief Introduction to SPICE

- ❑ SPICE = “Simulation Program with Integrated Circuit Emphasis”
- ❑ A general purpose program that simulates electronic circuits.
- ❑ *PSpice* = PC version of SPICE (from OrCAD Corporation)

Brief Introduction to SPICE

- Types of analysis supported:
 - DC sweeps of current/voltage sources (.DC)
 - operating point determination (.OP)
 - Thevenin equivalents (.TF)
 - time-domain (transient) response (.TRAN)
 - Fourier analysis (.FOUR)
 - small-signal frequency response (.AC)
 - noise analysis (.NOISE)
 - sensitivity analysis (.SENS)
 - etc.

General Procedure for Using SPICE

- 3 basic steps:

- 1) create a source file for the circuit to be simulated
- 2) enter the source file into the computer to run the program
- 3) instruct the computer to print our plot the results

- Educational version of PSpice is available for downloading free from the web site:

<http://www.orcad.com/Product/Simulation/PSpice/eval.asp>

General Procedure for Using SPICE

- For specific syntax of input file statements, consult the appropriate reference
- A few good references are:


[1] P. Tuinenga, *A Guide to Circuit Simulation and Analysis Using PSpice*, 2nd Ed., Englewood, NJ: Prentice Hall, 1992.

[2] S. Reidel and J. Nilsson, *Introduction to PSpice*, Menlo Park, CA: Addison Wesley, 1997.

[3] M. Rashid, *SPICE for Circuits and Electronics Using PSpice*, Englewood, NJ: Prentice Hall, 1995.

SPICE Example 1

- Consider the DC circuit below:

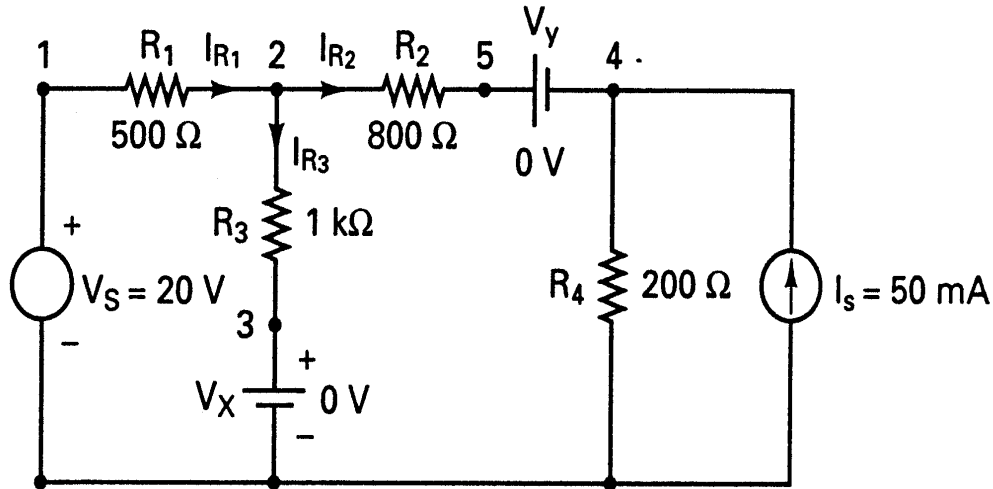

- Suppose we want to calculate and print all node voltages and the current and power of all voltage sources (V_S , V_X , and V_Y).

SPICE Example 1

Input File

- Must have five key parts:
 - 1) Title
 - 2) Circuit Description
 - 3) Analysis Requests
 - 4) Output Requests
 - 5) End of Program (.END)

SPICE Example 1

Sample Input File:

```
** DC Circuit Example 1 **
```

```
** Circuit Description **
```

```
VS 1 0 DC 20V ; DC voltage source of 20 volts
```

```
IS 0 4 DC 50MA ; DC current source of 50 milliamps
```

```
R1 1 2 500 ; Resistance of 500 ohms
```

```
R2 2 5 800 ; Resistance of 800 ohms
```

```
R3 2 3 1KOHM ; Resistance of 1 kilo-ohm
```

```
R4 4 0 200 ; Resistance of 200 ohms
```

```
** Analysis Requests **
```

```
VX 3 0 DC 0V ; Measures current through R3
```

```
VY 5 4 DC 0V ; Measures current through R2
```

```
** Output Requests **
```

```
.OP ; Directs the bias point to the output file
```

```
.END ; End of circuit file
```

SPICE Example 1

Running the program:

- ❑ Goto: Start -> Programs -> PSpice Student-> PSpice AD Student
- ❑ From “File” menu, goto: New -> Test File
- ❑ Type in your input file
- ❑ Save your input file with a .CIR extension
- ❑ From “Simulation” menu, goto Run *<input_file>*
 - The output file will automatically be given the extension:
<input_file>.OUT
 - The simulation results (i.e., plots) file will have the extension:
<input_file>.DAT

SPICE Example 1

Viewing program output:

- ❑ To view the output file:
 - From “View” menu, goto “Output File”

- ❑ To view the simulation results (i.e., plots):
 - From “View” menu, goto “Simulation Results”
 - From “Trace” menu, goto “Add Trace”
 - Select the desired voltage and/or current node

SPICE Example 1

Results appearing in <input_file>.OUT:

```
****      SMALL-SIGNAL BIAS SOLUTION      TEMPERATURE = 27.000 DEG C
NODE  VOLTAGE      NODE  VOLTAGE      NODE  VOLTAGE      NODE  VOLTAGE
(  1)  20.0000  (  2)  12.5000  (  3)   0.0000  (  4)  10.5000
(  5)  10.5000
VOLTAGE SOURCE CURRENTS
NAME      CURRENT
VS         -1.500E-02      IR1 = 15 mA
VX         1.250E-02      IR3 = 12.5 mA
VY         2.500E-03      IR2 = 2.5 mA
TOTAL POWER DISSIPATION  3.00E-01 WATTS
JOB CONCLUDED
TOTAL JOB TIME          1.04
```

SPICE Example 2

- For the same circuit, suppose we want to calculate and print the voltage at node 4, and the currents through R_2 and R_3 for $V_S = 10\text{ V}$, 20 V , and 30 V .

- *Solution:*

1. The input file is the same as above, except that the .OP statement is replaced by:

```
.DC VS 10V 30V 10V ; Sweep VS from 10 V to 30V in 10V  
increments
```

and after that, we add one additional statement:

```
.PRINT DC V(4) I(VX) I(VY) ; Prints the results of the DC  
sweep
```

SPICE Example 2

New Input File:

```
** DC Circuit Example 2 **
```

```
** Circuit Description **
```

```
VS 1 0 DC 20V ; DC voltage source of 20 volts  
IS 0 4 DC 50MA ; DC current source of 50 milliamps  
R1 1 2 500 ; Resistance of 500 ohms  
R2 2 5 800 ; Resistance of 800 ohms  
R3 2 3 1KOHM ; Resistance of 1 kilo-ohm  
R4 4 0 200 ; Resistance of 200 ohms
```

```
** Analysis Requests **
```

```
VX 3 0 DC 0V ; Measures current through R3  
VY 5 4 DC 0V ; Measures current through R2
```

```
** Output Requests **
```

```
.DC VS 10V 30V 10V  
.PRINT DC V(4) I(VX) I(VY)  
.END ; End of circuit file
```


SPICE Example 2

Solution (cont).

2. The program is run in the same way as above (except that we might want to use a different name for our new *input_file*).
3. The resulting <input_file>.out now looks like:

```
****      DC TRANSFER CURVES                TEMPERATURE = 27.000 DEG C
VS          V(4)          I (VX)          I (VY)
1.000E+01   9.500E+00     7.500E-03   -2.500E-03
2.000E+01   1.050E+01     1.250E-02   2.500E-03
3.000E+01   1.150E+01     1.750E-02   7.500E-03
          JOB CONCLUDED
          TOTAL JOB TIME                1.21
```

SPICE Example 3

□ For the same circuit, suppose we want to calculate and *plot* the current through R_2 for $V_S = 10\text{ V}$, 30 V , and 50 V .

□ *Solution:*

1. The input file is the same as Example 1, except that the `.OP` statement is replaced by:

```
.DC VS 10V 50V 20V ; Sweep VS from 10 V to 50V in 20V  
increments
```

```
.PLOT DC I(VY) ; Plots the results of the DC sweep
```

```
.PROBE ; Invokes PSPICE graphical waveform analyzer
```

SPICE Example 3

New Input File:

```
** DC Circuit Example 3 **
```

```
** Circuit Description **
```

```
VS 1 0 DC 20V ; DC voltage source of 20 volts  
IS 0 4 DC 50MA ; DC current source of 50 milliamps  
R1 1 2 500 ; Resistance of 500 ohms  
R2 2 5 800 ; Resistance of 800 ohms  
R3 2 3 1KOHM ; Resistance of 1 kilo-ohm  
R4 4 0 200 ; Resistance of 200 ohms
```

```
** Analysis Requests **
```

```
VX 3 0 DC 0V ; Measures current through R3  
VY 5 4 DC 0V ; Measures current through R2
```

```
** Output Requests **
```

```
.DC VS 10V 50V 20V  
.PLOT DC I(VY)  
.PROBE  
.END ; End of circuit file
```

SPICE Example 3

2. The program is run in the same way as above, except that we now want to view the simulation results using the “Trace” menu.
3. The desired plot looks like:

