

NAME: _____

GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

ECE 4430
Fall 2002

Second Exam
October 30, 2002

Closed Book and Notes

General Instructions:

1. Write on one side of the paper. (1 Pt.)
2. Put answers to all questions in the spaces provided on the test. (1 Pt.)
3. Show all work for full credit on questions requiring calculations. No credit will be given for answers alone, without supporting work.
4. Problems and questions are weighted as indicated. The maximum score is 100 points.
5. If you need more paper (provided in class), remove the staple from the exam and, when finished, arrange the test in order. Place the extra pages with supporting work in the test behind the page where the problem appears and indicate accordingly. Staple the entire test together so that there are no loose pages. (1 Pt.)

TEST SCORE: _____ / 100

I certify that I have neither given nor received any assistance while taking this test from anyone.

_____ (Signature) (1 Pt.)

Place a check mark in the box if you observed any suspicious actions while taking this test.

Formula Sheet: Equations/Constants that you may, or may not, need are listed below:

$$K' = 50 \mu\text{A}/\text{V}^2 \text{ (unless otherwise stated in the problem)}$$

$$K_n = K' W/L$$

$$\lambda = 0.01 \text{ V}^{-1} \text{ (unless otherwise stated in the problem)}$$

$$V_{TO} = 0.7 \text{ V (unless otherwise stated in the problem)}$$

$$\gamma = 0.5 \text{ V}^{1/2} \text{ (unless otherwise stated in the problem)}$$

$$2\phi_F = 0.6 \text{ V (unless otherwise stated in the problem)}$$

$$I_{D\text{-Triode}} = (K_n/2) [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$I_{D\text{-Sat}} = (K_n/2) (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$$V_{TN} = V_{TO} + \gamma [\text{sqrt}(2\phi_F - V_{BS}) - \text{sqrt}(2\phi_F)]$$

$$r_{o\text{-MOS}} \approx 1 / (\lambda I_{DS})$$

$$g_{m\text{-MOS}} = \text{sqrt}[2I_{DS}K_n]$$

$$V_{ds\text{-sat}} = \text{sqrt}(2I_{DS}/K_n)$$

$$g_{mb\text{-MOS}} = \eta g_{m\text{-MOS}}$$

$$\eta = \gamma \div 2 \text{ sqrt}(2\phi_F - V_{BS})$$

$$V_t = kT/q \approx 26 \text{ mV and } I_S = 1\text{E-}15 \text{ A (unless otherwise stated in the problem)}$$

$$I_{D\text{diode}} = I_S [\exp(V_D/V_t) - 1]$$

$$C_j = \frac{C_{j0}}{\left(1 - \frac{V_D}{\psi_0}\right)^m} \quad \rightarrow 0.33 \leq m \leq 0.5$$

$$V_A = 100 \text{ V (unless otherwise stated in the problem)}$$

$$\beta_F = 50 \text{ (unless otherwise stated in the problem)}$$

$$I_{CE} = I_S [\exp(V_{BE}/V_t) - 1] [1 + V_{CE}/V_A]$$

$$r_{o\text{-NPN}} = V_A / I_{CE}$$

$$g_{m\text{-NPN}} = I_{CE}/V_t$$



$$\text{CMRR} = |A_{dm}| / |A_{cm}|$$

$$Z_{\text{miller-in}} = Z / (1 - k)$$


$$Z_{\text{miller-out}} = Z k / (k - 1)$$

Fabrication – Part A (30 Points)

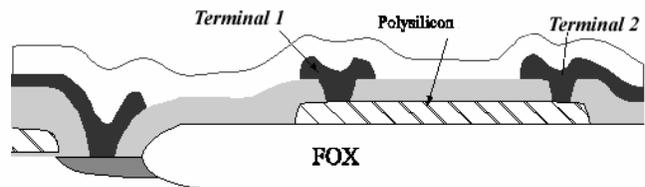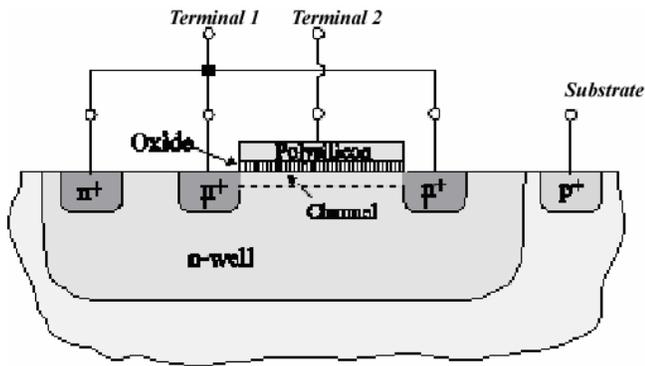1. Draw the schematic (label the terminals) and identify the devices of the figures shown below, as they would be used (be specific – base-emitter diode of lateral NPN, accumulation-mode MOS capacitor, etc.). (10 pts)




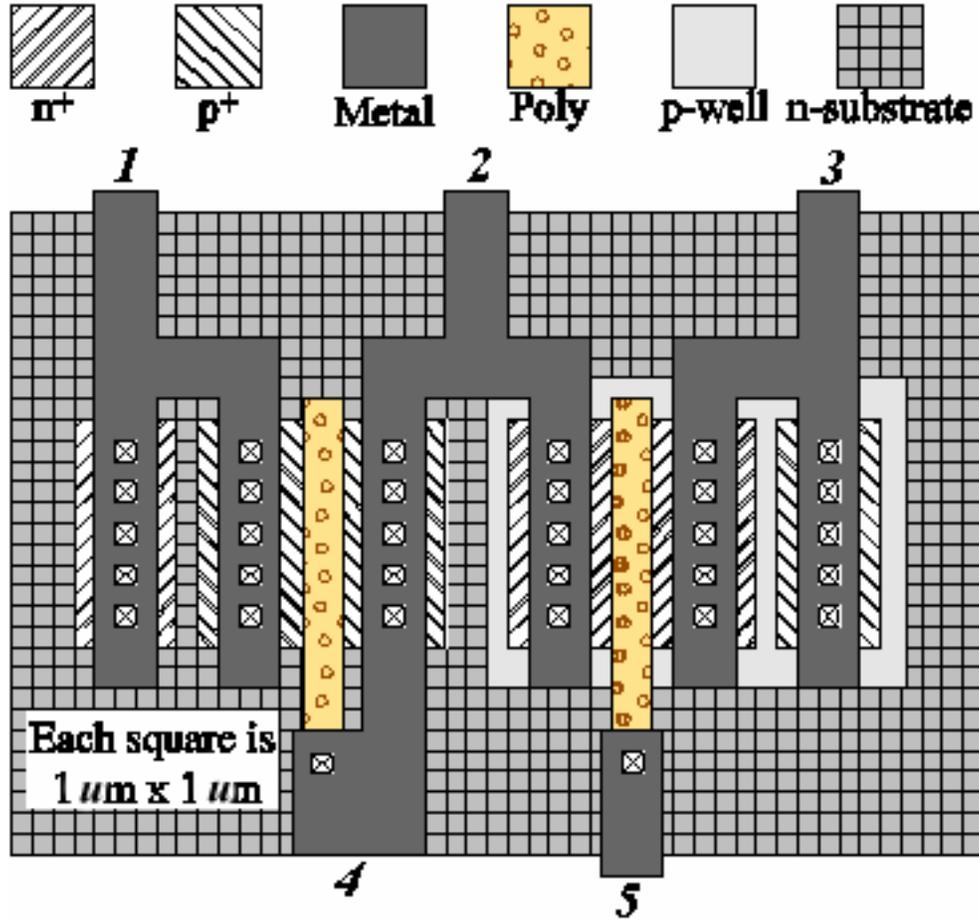2. Use the layout shown below to answer the following questions.



(a) Draw the corresponding schematic.

(5 pts)

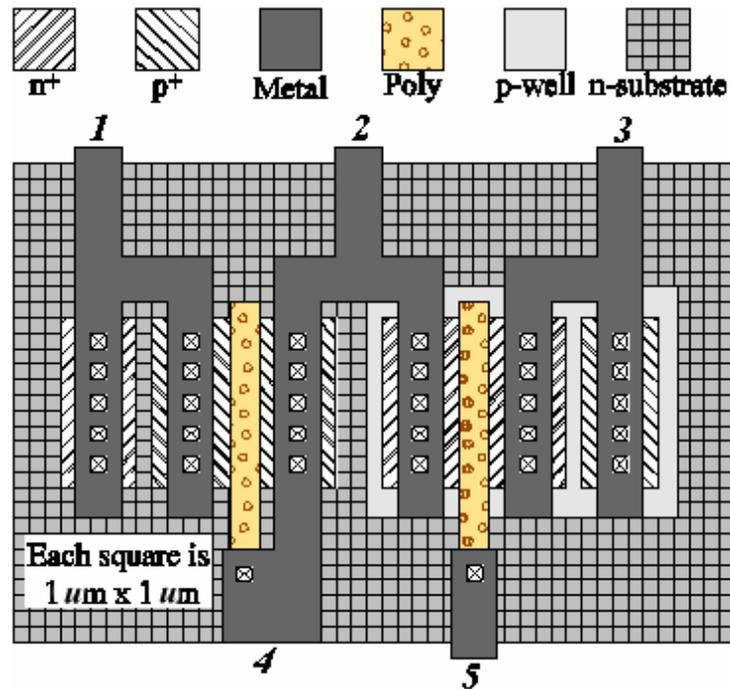

(b) Which terminal(s) (1, 2, 3, 4, or 5) is(are) more than likely connected to the positive power supply?

_____ (2 pts)

Why? _____

_____ (2 pts)

(c) Which terminal(s) is(are) more than likely connected to the negative power supply?

_____ (2 pts)

Why? _____

_____ (2 pts)

(d) Which terminal(s) is(are) more than likely the input(s) of the circuit?

_____ (2 pts)

(e) What specific capacitor components (e.g., $C_{db_sidewall}$, C_{db_bottom} , $C_{gs_overlap}$, $C_{gs_saturation}$, etc.) do you


expect to be present on terminal 5? (5 pts)

Single and Two Transistor Amplifiers – Part B (25 Points)

1. Circle the single transistor amplifiers that produce a non-inverting transfer function. (6 pts)

CC CB CE CD CG CS

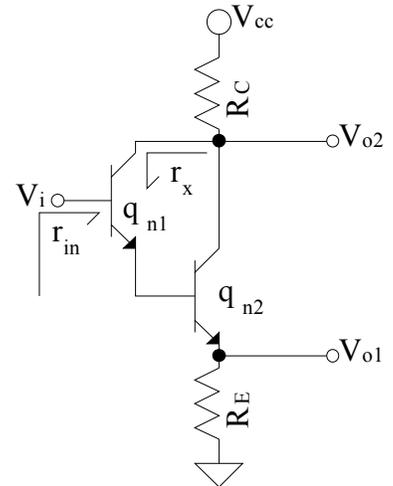2. For the circuit shown and using small signal parameters (e.g., r_{π} , g_m , β , etc.), (a) derive input resistance r_{in} and the transfer function from V_i to V_{o1} (i.e., V_{o1}/V_i) –assume V_A is infinite (r_o is infinite).




(10 pts)

(b) The gain from V_i to V_{o2} (i.e., V_{o2}/V_i) is **greater than / less than / equal to** V_{o1}/V_i . (2 pts)


(c) **True / False**: V_{o1} is in phase with V_{o2} . (2 pts)

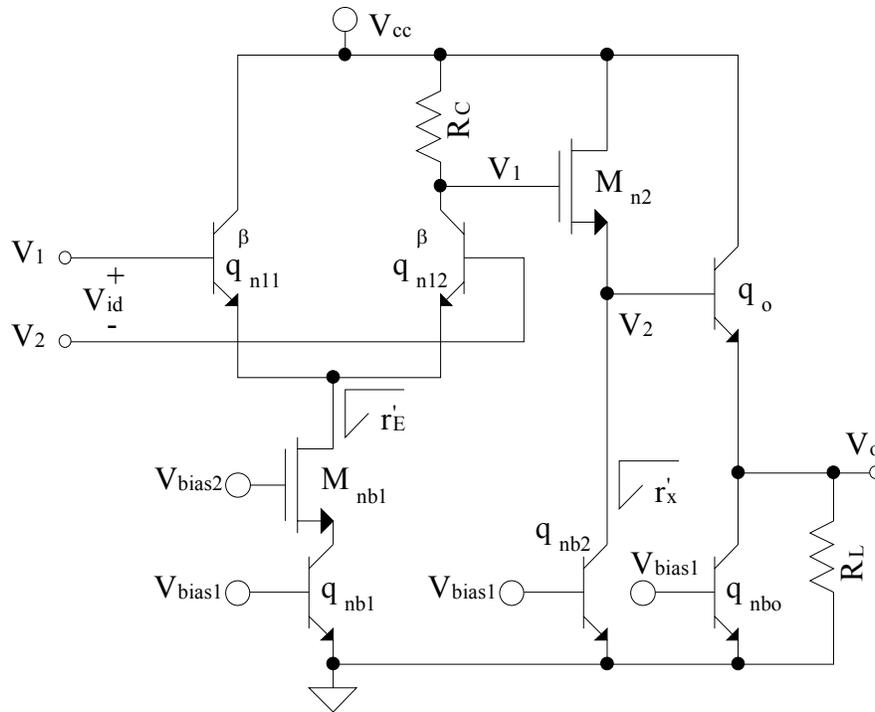(d) Derive the resistance looking into the collector of q_{n1} (r_x)? (5 pts)



2. Which devices have been used as current sources or sinks? _____ (6 pts)
3. Of those, which one(s) exhibit(s) the lowest V_{min} ? _____ (6 pts)
4. Which one(s) has(ve) the best output resistance performance? _____ (4 pts)

Part A. ① ②

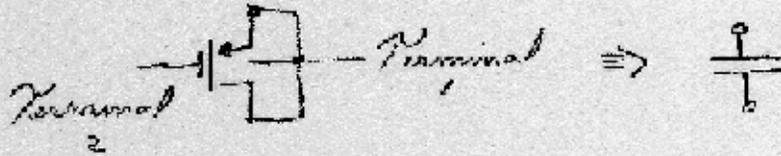

MOS Capacitor


③ Terminal 2



Terminal 1

Polysilicon Resistor

④ n-well, p-well Technology


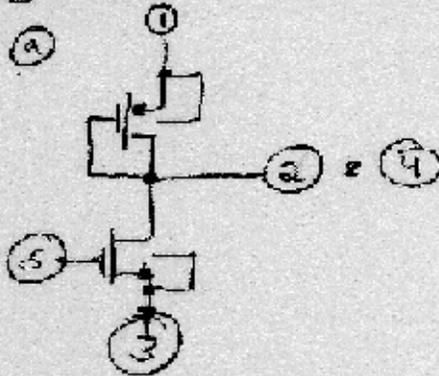


① ① \Rightarrow Reverse bias n-well-substrate junction diodes, thereby isolating all currents sharing the same substrate

③ ③ \Rightarrow Isolate p-well from substrate \Rightarrow reverse-bias p-well-substrate diode


④ ⑤

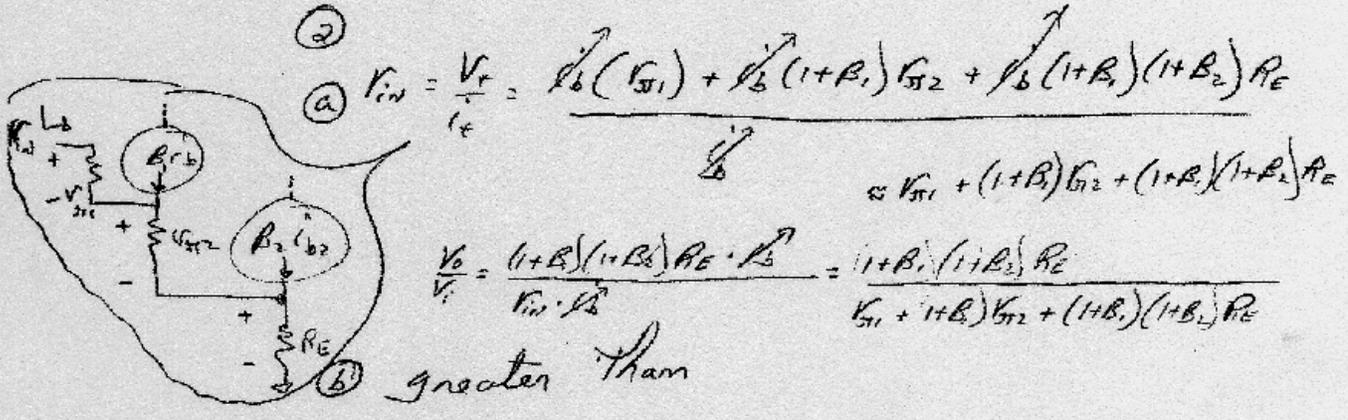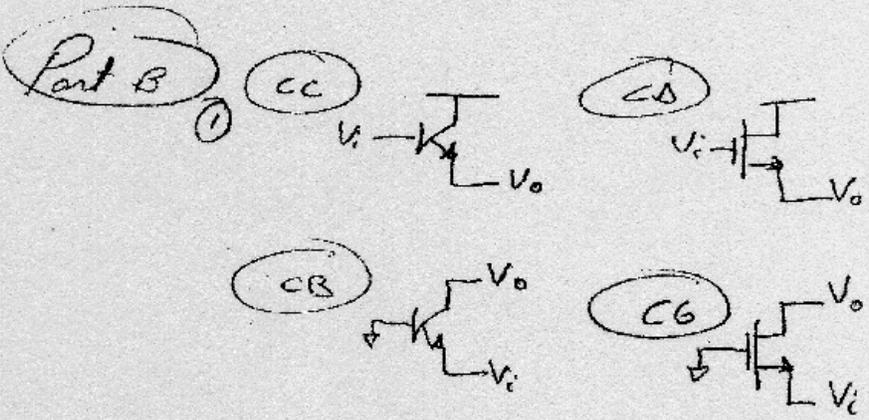Part A (E) $C_s = C_{gs-saturation} + C_{gs-overlap} + C_{g-overlap}$ & $C_{gs-saturation} = \frac{2}{3} C_{ox}'' WL$ (2)



(c) False

(d)

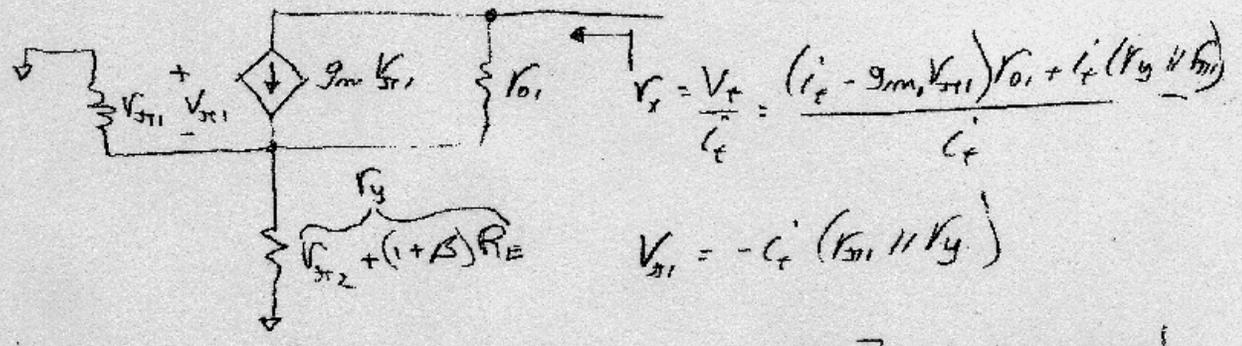

$\therefore V_x = \frac{[i_r + i_r g_{m1} (r_{pi1} || r_{pi2})] r_{o1} + i_r (r_{pi2} || r_{pi1})}{i_r}$

$\therefore V_x = [1 + g_{m1} (r_{pi1} || r_{pi2})] r_{o1} + (r_{pi2} || r_{pi1}) \approx g_{m1} [(r_{pi2} + (1+B) R_E) || r_{pi1}] r_{o1}$

③

Part B ① ② cont.

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{\beta V_E}{I_{C1}} = \frac{\beta V_E}{I_{C2}} = \beta r_{\pi 2}$$


$$g_{m1} = \frac{I_{C1}}{V_E} = \frac{I_{C2}}{\beta V_E} = \frac{g_{m2}}{\beta}$$

$$r_{o1} = \frac{V_{A1}}{I_{C1}} = \frac{V_{A2}}{I_{C2}} = \beta r_{o2}$$

$$\therefore V_x \approx \left(\frac{g_{m2}}{\beta} \right) \beta r_{o2} \left[r_{\pi 2} + (1+\beta) R_E \right] \parallel \beta r_{o2}$$

Part C


a

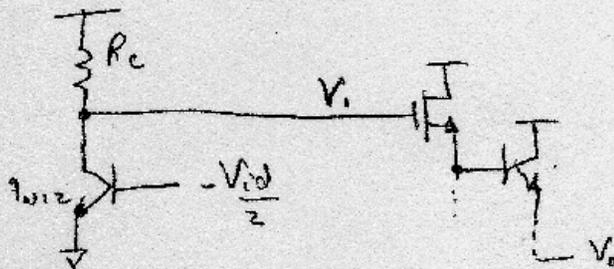


$$\frac{V_i}{V_{id}} = - \left(- \frac{g_m R_C}{2} \right)$$

$$\frac{V_o}{V_{id}} = \frac{V_i}{V_{id}} \frac{V_o}{V_i} = \frac{g_m R_C}{2} (1) = \frac{g_m R_C}{2}$$

b

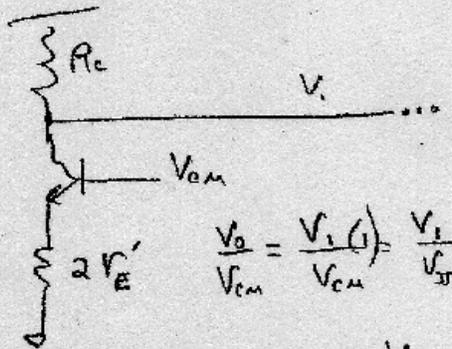
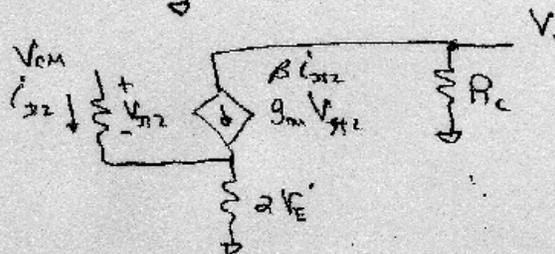
$$\frac{V_o}{V_{em}} = \frac{V_i (1)}{V_{em}} = \frac{V_i}{V_{\pi 12}} \frac{V_{\pi 12}}{V_{em}} = (g_m R_C) \left(\frac{\beta r_{\pi}}{\beta r_{\pi} + (1+\beta) 2R'_E} \right)$$



$$= \frac{g_m R_C \beta r_{\pi}}{\beta r_{\pi} + (1+\beta) 2R'_E}$$

$$\approx \frac{g_m R_C}{1 + (1+\beta) \frac{2R'_E}{\beta r_{\pi}}}$$

Part c

②

$$CMRR = \frac{|A_{dm}|}{|A_{cm}|} = \left(\frac{g_m r_c}{2} \right) \left(\frac{1 + \frac{(1+\beta) 2r_e}{r_{\pi}}}{g_m r_c} \right) \quad (4)$$

$$\approx \left(\frac{1+\beta}{r_{\pi}} \right) r_e \approx g_m r_e$$

Part c

② M_{vb1} and g_{vb1} g_{vb2} g_{vb0} ③ g_{vb2} g_{v0} ④ M_{vb1} and g_{vb1}